

## Equations to Know

### Chapter 26

Terminal Voltage

$$V_{ab} = \mathcal{E} - Ir$$

Charging a battery

$$V_{ab} = \mathcal{E} + Ir$$

Resistance in Series

$$R_{eq} = R_1 + R_2 + R_3 \dots$$

Resistance in Parallel

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \dots$$

Homicha's Rule

$$R_x R_1 = R_2 R_3$$

RC Circuit: Time Constant

$$\tau = RC$$

RC Circuit: Charge on a Charging Capacitor

$$Q = C\mathcal{E} \left( 1 - e^{-\frac{t}{RC}} \right)$$

RC Circuit: Voltage across a Charging Capacitor

$$V_C = \mathcal{E} \left( 1 - e^{-\frac{t}{RC}} \right)$$

RC Circuit: Voltage across a Resistor (Charging Capacitor)

$$V_R = \mathcal{E} e^{-\frac{t}{RC}}$$

RC Circuit: Current in a Resistor (Charging Capacitor)

$$I = \frac{\mathcal{E}}{R} e^{-\frac{t}{RC}}$$

RC Circuit: Charge on a Discharging Capacitor

$$Q = Q_0 e^{-\frac{t}{RC}}$$

RC Circuit: Voltage across a Discharging Capacitor

$$V_C = V_0 e^{-\frac{t}{RC}}$$

RC Circuit: Voltage across a Resistor (Discharging Capacitor)

$$V_R = \mathcal{E} e^{-\frac{t}{RC}}$$

RC Circuit: Current in a Resistor (Discharging Capacitor)

$$I = I_0 e^{-\frac{t}{RC}}$$

Galvanometer used as an Ammeter (Figure 26-23)

$$I_R R_{sh} = I_G r$$

Galvanometer used as a Voltmeter (Figure 26-24)

$$V = I_{full-scale} (r + R_{ser})$$